

Sequential Logic Circuit Design Module III

Flip-Flop Conversion

The FF conversion is a process to design a new FF from the available FF.

Step-by-step procedure for FF conversion

- [1] Identify available and required FFs.
- [2] Make characteristic table for required FF.
- [3] Make excitation table for available FF.
- [4] Write boolean expression for available FF in terms of required FF.
- [5] Draw the logic diagram.

SR FF to D FF Conversion

Digital Logic
Design

Flip- Flop
Conversion

Problems on
FF Conversion

Step-1: Available FF : **SR**
Required FF : **D**

SR FF to D FF Conversion

Step-1: Available FF : **SR**
Required FF : **D**

Step-2-3: Characteristic (**D**)
and excitation (**SR**) table

D	Q_n	Q_{n+1}	S	R
0	0	0	0	×
0	1	0	0	1
1	0	1	1	0
1	1	1	×	0

SR FF to D FF Conversion

Step-1: Available FF : **SR**
Required FF : **D**

Step-2-3: Characteristic (**D**)
and excitation (**SR**) table

D	Q_n	Q_{n+1}	S	R
0	0	0	0	×
0	1	0	0	1
1	0	1	1	0
1	1	1	×	0

Step-4: Boolean expression

$$S = D$$

$$R = \bar{D}$$

SR FF to D FF Conversion

Step-1: Available FF : **SR**
Required FF : **D**

Step-2-3: Characteristic (**D**)
and excitation (**SR**) table

D	Q_n	Q_{n+1}	S	R
0	0	0	0	×
0	1	0	0	1
1	0	1	1	0
1	1	1	×	0

Step-4: Boolean expression

D \ Q_n	0	1
0	0	0
1	1	X


$S = D$

D \ Q_n	0	1
0	X	1
1	0	0

$R = \bar{D}$

Step-5: Circuit Diagram

Logic Diagram

 

SR FF to T FF Conversion

Digital Logic
Design

Flip- Flop
Conversion

Problems on
FF Conversion

Step-1: Available FF : **SR**

Required FF : **T**

SR FF to T FF Conversion

Step-1: Available FF : **SR**

Required FF : **T**

Step-2-3: Characteristic (T)
and excitation (SR) table

T	Q_n	Q_{n+1}	S	R
0	0	0	0	×
0	1	1	×	0
1	0	1	1	0
1	1	0	0	1


SR FF to T FF Conversion

Step-1: Available FF : **SR**

Step-2-3: Characteristic (T) and excitation (SR) table


T	Q_n	Q_{n+1}	S	R
0	0	0	0	×
0	1	1	×	0
1	0	1	1	0
1	1	0	0	1

Step-4: Boolean expression

 

Required FF : **T**


Step-5: Circuit Diagram

 

SR FF to JK FF

Step-1: Available FF : **SR**
Required FF : **JK**

Step-5: Circuit Diagram

 

Step-2-3: Characteristic and excitation table

J	K	Q_n	Q_{n+1}	S	R
0	0	0	0	0	×
0	0	1	1	×	0
0	1	0	0	0	×
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	1	×	0
1	1	0	1	1	0
1	1	1	0	0	1

Step-4: Boolean expression

For S					For R				
J \ KQ	00	01	11	10	J \ KQ	00	01	11	10
0	0	X	0	0	0	X	0	1	X
1	1	X	0	1	1	0	0	1	0

JK'

KQ


JK FF to SR FF Conversion

J-K Flip Flop to S-R Flip Flop

Conversion Table

S-R Inputs		Outputs		J-K Inputs	
S	R	Qp	Qp+1	J	K
0	0	0	0	0	X
0	0	1	1	X	0
0	1	0	0	0	X
0	1	1	0	X	1
1	0	0	1	1	X
1	0	1	1	X	0
1	1	Invalid		Dont care	
1	1	Invalid		Dont care	

Logic Diagram

 

S	RQp			
	00	01	11	10
0	0 ⁰	X ¹	X ³	0 ²
1	X ⁴	X ⁵	X ⁷	X ⁶

J=S

S	RQp			
	00	01	11	10
0	X ⁰	0 ¹	1 ³	X ²
1	X ⁴	0 ⁵	X ⁷	X ⁶

K-maps

K=R

Home Assignment on FF Conversion

Digital Logic
Design

Flip- Flop
Conversion

Problems on
FF Conversion

- JK Flip Flop to D Flip Flop
- JK Flip Flop to T Flip Flop
- D Flip Flop to SR Flip Flop
- D Flip Flop to JK Flip Flop
- D Flip Flop to T Flip Flop
- T Flip Flop to SR Flip Flop
- T Flip Flop to JK Flip Flop
- T Flip Flop to D Flip Flop

Problem 1 on FF Conversion

A new clocked X-Y flip-flop is defined with two inputs, X and Y is in addition to the clock input. The flip flop functions as follows:

- 1 If $XY = 00$, the FF changes state with each clock pulse
- 2 If $XY = 01$, the FF state Q becomes '1' with the next clock pulse
- 3 If $XY = 10$, the FF state Q becomes '0' with the next clock pulse
- 4 If $XY = 11$, the same state occurs with the clock pulse.

- (a) Write the truth table for the XY FF.
- (b) Write the excitation table for the XY FF.
- (c) Convert JK FF into XY FF by adding some external gates.

Solution of problem 1

Table: (a) Truth Table for XY FF

X	Y	Q_{n+1}
0	0	Q'_n
0	1	1
1	0	0
1	1	Q_n

Table: (b) Excitation Table for XY Flip Flop

Q_n	Q_{n+1}	J	K
0	0	1	×
0	1	0	×
1	0	×	0
1	1	×	1


Table: Characteristic Table for XY Flip Flop

X	Y	Q_n	Q_{n+1}
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Now follow the same procedure that we did in the standard FF conversion

 
Problem 2 on FF Conversion

A sequential circuit using D FF and logic gates is shown in figure, where X and Y are the inputs and Z is output. The circuit is



 Problem 2 on FF Conversion

A sequential circuit using D FF and logic gates is shown in figure, where X and Y are the inputs and Z is output. The circuit is



a S-R FF with inputs $X=R$ and $Y=S$

b S-R FF with inputs $X=S$ and $Y=R$

c J-K FF with inputs $X=J$ and $Y=K$

d **J-K FF with inputs $X=K$ and $Y=J$**

Solution of problem 2

From the Circuit: $D = X'Z + YZ'$

Output $Z = Q = D$

Inputs are X and Y

X	Y	$Q_n = Z$	$Q_{n+1} = D$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

Solution of problem 2

From the Circuit: $D = X'Z + YZ'$

Output $Z = Q = D$

Inputs are X and Y

X	Y	$Q_n = Z$	$Q_{n+1} = D$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

Table: JK Flip Flop

J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	\bar{Q}_n

The answer is [d] J-K FF with inputs $X=K$ and $Y=J$