

Sequential Logic Circuit Design Module III (Lec-2)

SR Latch

 


Figure: SR Latches using NOR and NAND Gates

SR Latch is a circuit with:

- Two cross-coupled NOR gate or 2 cross-coupled NAND gate.

SR Latch

 


Figure: SR Latches using NOR and NAND Gates

SR Latch is a circuit with:

- Two cross-coupled NOR gate or 2 cross-coupled NAND gate.
- Two inputs S for SET and R for RESET.

SR Latch

 


Figure: SR Latches using NOR and NAND Gates

SR Latch is a circuit with:

- Two cross-coupled NOR gate or 2 cross-coupled NAND gate.
- Two inputs S for SET and R for RESET.
- Two outputs Q , Q' . Both outputs are complement to each other.

SR Latch using NAND Gates

 


Table: Truth Table for SR Latch

S	R	Q
0	0	Invalid state
0	1	1
1	0	0
1	1	Previous state

Figure: Logic Diagram of SR Latch

SR Latch using NAND Gates

 


Table: Truth Table for SR Latch

S	R	Q
0	0	Invalid state
0	1	1
1	0	0
1	1	Previous state

Figure: Logic Diagram of SR Latch

- When both inputs $S = R = 0$, the outputs Q and $Q' = 1$.

SR Latch using NAND Gates

 


Table: Truth Table for SR Latch

S	R	Q
0	0	Invalid state
0	1	1
1	0	0
1	1	Previous state

Figure: Logic Diagram of SR Latch

- When both inputs $S = R = 0$, the outputs Q and $Q' = 1$.
- The valid states only when $(Q = 0, \text{ and } Q' = 1)$ or $(Q = 1, \text{ and } Q' = 0)$.

SR Latch using NOR Gates

 


Table: Truth Table for SR Latch

S	R	Q
0	0	Previous state
0	1	0
1	0	1
1	1	Invalid state

Figure: Logic Diagram of SR Latch

SR Latch using NOR Gates

 


Table: Truth Table for SR Latch

S	R	Q
0	0	Previous state
0	1	0
1	0	1
1	1	Invalid state

Figure: Logic Diagram of SR Latch

- When both inputs $S = R = 1$, the outputs Q and $Q' = 0$.

SR Latch using NOR Gates

 


Table: Truth Table for SR Latch

S	R	Q
0	0	Previous state
0	1	0
1	0	1
1	1	Invalid state

Figure: Logic Diagram of SR Latch

- When both inputs $S = R = 1$, the outputs Q and $Q' = 0$.
- The truth table of NOR latch is opposite to the NAND latch.

Flip Flop

- Flip flop is a basic memory element, which can store one bit of data.

Flip Flop

- Flip flop is a basic memory element, which can store one bit of data.
- Flip flop have two stable states, that's why it is called ad bistable multivibrator.

Flip Flop

- Flip flop is a basic memory element, which can store one bit of data.
- Flip flop have two stable states, that's why it is called ad bistable multivibrator.
- Flip flop is an edge triggered circuit.

Flip Flop

- Flip flop is a basic memory element, which can store one bit of data.
- Flip flop have two stable states, that's why it is called ad bistable multivibrator.
- Flip flop is an edge triggered circuit.

Flip Flops Classification

[1] SR Flip Flop

[3] D Flip Flop

[2] JK Flip Flop

[4] T Flip Flop

Flip Flop

- Flip flop is a basic memory element, which can store one bit of data.
- Flip flop have two stable states, that's why it is called ad bistable multivibrator.
- Flip flop is an edge triggered circuit.

Flip Flops Classification

[1] SR Flip Flop

[3] D Flip Flop

[2] JK Flip Flop

[4] T Flip Flop

Procedure for Designing of Flip Flops

[1] Truth Table

[3] Characteristic Equation

[2] Characteristic Table

[4] Excitation Table

SR Flip Flop


 


Table: Truth Table for SR Flip Flop

Clk	S	R	Q
0	×	×	Previous state
1	0	0	Previous state
1	0	1	0 (Reset State)
1	1	0	1 (Set State)
1	1	1	Invalid state

SR Flip Flop

Table: Truth Table for SR Flip Flop

 


Clk	S	R	Q
0	×	×	Previous state
1	0	0	Previous state
1	0	1	0 (Reset State)
1	1	0	1 (Set State)
1	1	1	Invalid state

- The control input (E or Clk) acts as an enable signal or clocked pulse for the two inputs.

SR Flip Flop

Table: Truth Table for SR Flip Flop

 

Clk	S	R	Q
0	×	×	Previous state
1	0	0	Previous state
1	0	1	0 (Reset State)
1	1	0	1 (Set State)
1	1	1	Invalid state

- The control input (E or Clk) acts as an enable signal or clocked pulse for the two inputs.
- When **E=0**, the circuit remains in the previous state.
- When **E goes to 1**, information from the S or R input is allowed to get the output.

SR Flip Flop

Table: Characteristic Table
for SR Flip Flop

S	R	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	×
1	1	1	×

SR Flip Flop

Table: Characteristic Table
for SR Flip Flop

S	R	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	×
1	1	1	×

Table: Excitation Table for SR
Flip Flop

Q_n	Q_{n+1}	S	R
0	0	0	×
0	1	1	0
1	0	0	1
1	1	×	0


SR Flip Flop

Table: Characteristic Table
for SR Flip Flop

S	R	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	×
1	1	1	×

Table: Excitation Table for SR
Flip Flop

Q_n	Q_{n+1}	S	R
0	0	0	×
0	1	1	0
1	0	0	1
1	1	×	0

 

K Map

SR Flip Flop

Table: Characteristic Table
for SR Flip Flop

S	R	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	×
1	1	1	×

Characteristic Equation

$$Q_{n+1} = S + \bar{R}Q_n$$

Table: Excitation Table for SR
Flip Flop

Q_n	Q_{n+1}	S	R
0	0	0	×
0	1	1	0
1	0	0	1
1	1	×	0

	$\bar{S}\bar{R}$	$\bar{S}R$	SR	$S\bar{R}$
\bar{Q}_n			X	1
Q_n	1		X	1

K Map